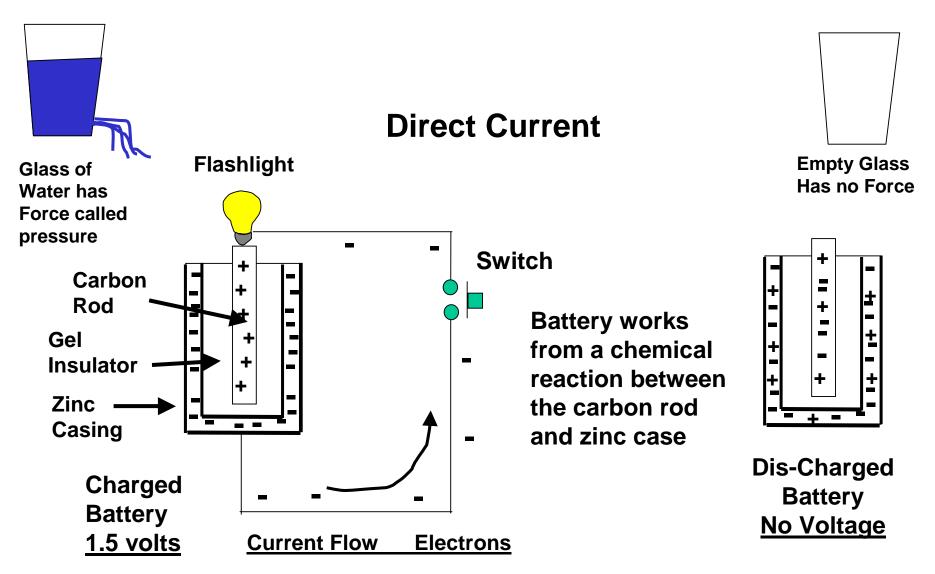
Electricity Merit Badge DC Direct Current




Voltage is the quantity of <u>electrical force</u> Measured in Volts

Current is the flow of <u>electrons</u> Measured in Amps

DC Stand for <u>Direct Current</u>


DC is current flowing in <u>one</u> direction

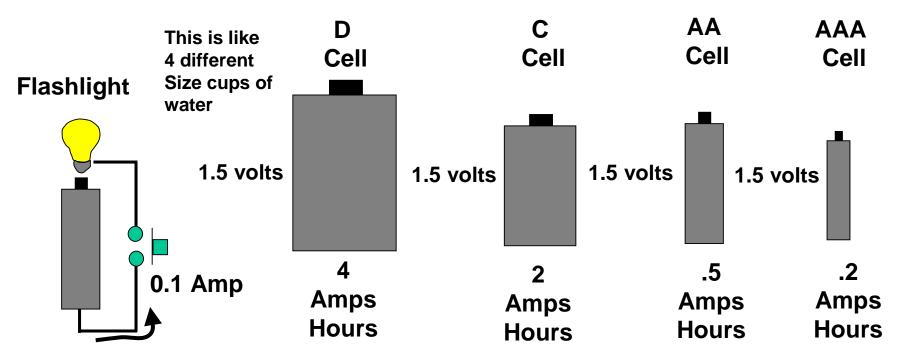Direct Current Pass out Typical Battery Rating - How Long will they Last



If a flashlight pulls .1 Amp, how long will each battery last? Time = Amp Hours / Load in Amps

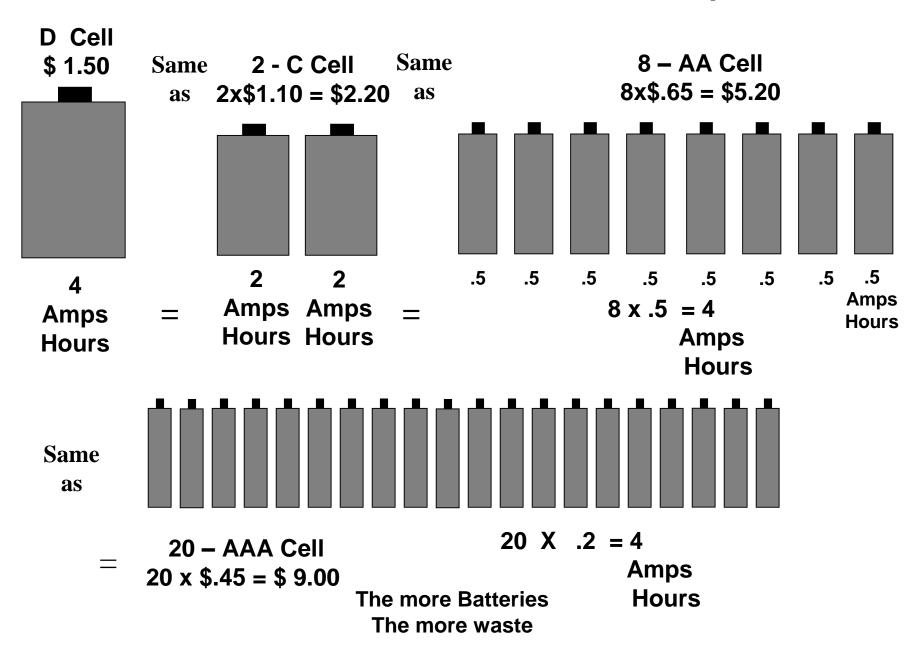
Direct Current Cost of Batteries for the Same Output




Many Battery Types

- •Zinc-carbon battery Also known as a standard carbon battery, zinc-carbon chemistry is used in all inexpensive AA, C and D dry-cell batteries. The electrodes are zinc and carbon, with an acidic paste between them that serves as the electrolyte.
- •Alkaline battery Used in common Duracell and Energizer batteries, the electrodes are zinc and manganese-oxide, with an alkaline electrolyte.
- •Lithium photo battery Lithium, lithium-iodide and lead-iodide are used in cameras because of their ability to supply power surges
- •Lead-acid battery Used in automobiles, the electrodes are made of lead and lead-oxide with a strong acidic electrolyte (rechargeable).
- •Nickel-cadmium battery The electrodes are nickel-hydroxide and cadmium, with potassium-hydroxide as the electrolyte (rechargeable).
- •Nickel-metal hydride battery This battery is rapidly replacing nickel-cadmium because it does not suffer from the memory effect that nickel-cadmiums do (rechargeable).
- •Lithium-ion battery With a very good power-to-weight ratio, this is often found in high-end laptop and cell phones (rechargeable).
- •Zinc-air battery This battery is lightweight and rechargeable.
- •Zinc-mercury oxide battery This is often used in hearing-aids.
- •Silver-zinc battery This is used in aeronautical applications because the power-to-weight ratio is good.
- Metal-chloride battery This is used in electric vehicles

Flashlight Diagram

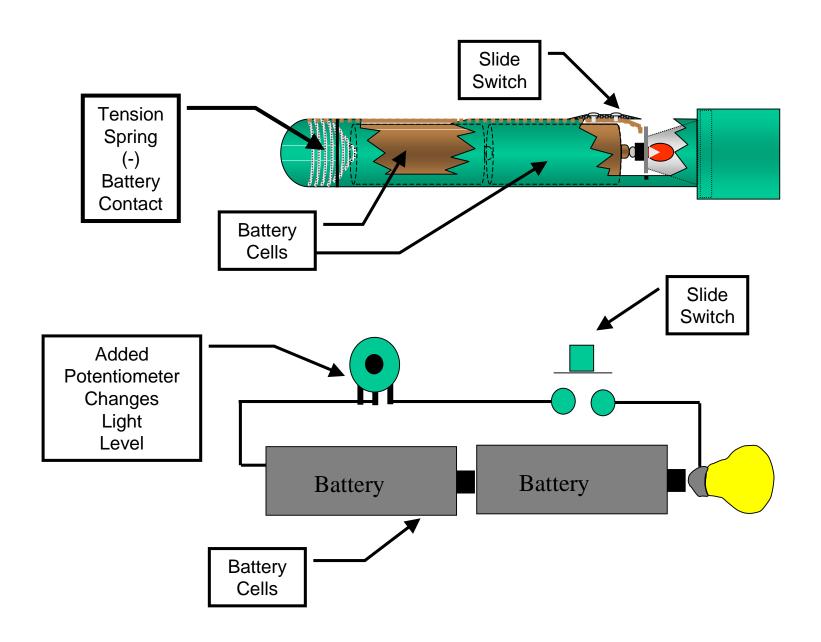


Car DC Electrical System

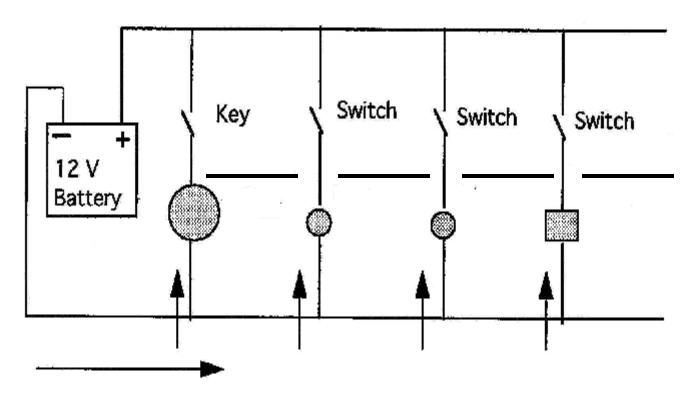


Name four electrical items in a car

Build an Electrical Switch

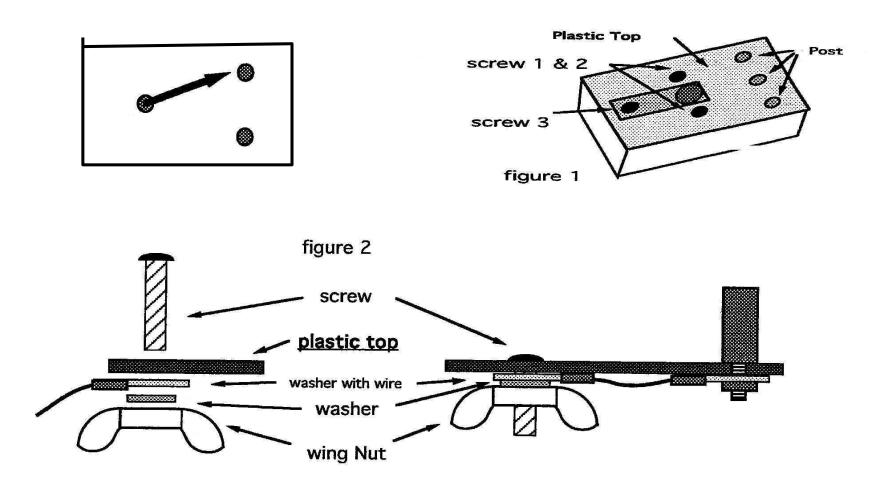


Build an Electrical Switch

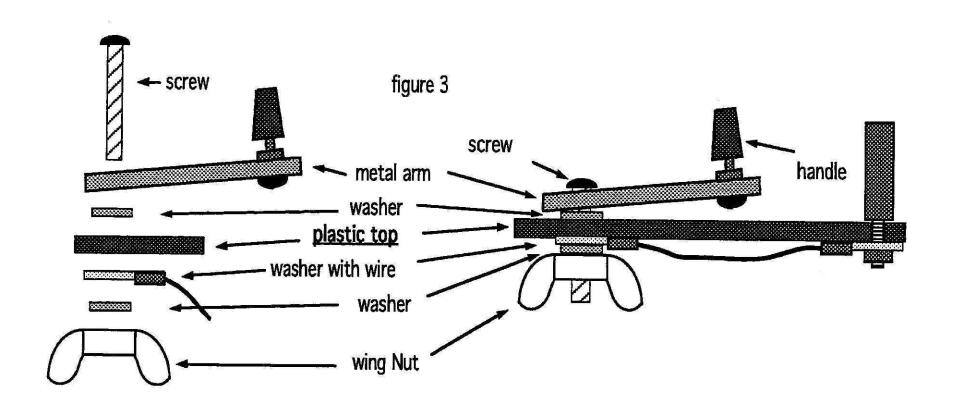


Direct Current Test Box

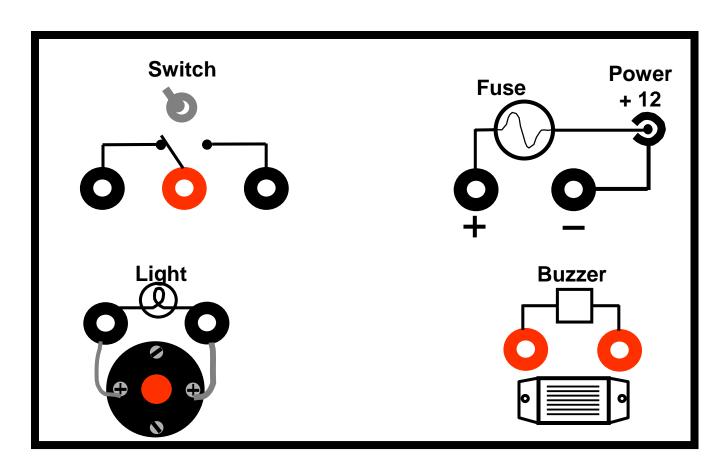Draw 4 different wiring test circuits, then pass out boxes.




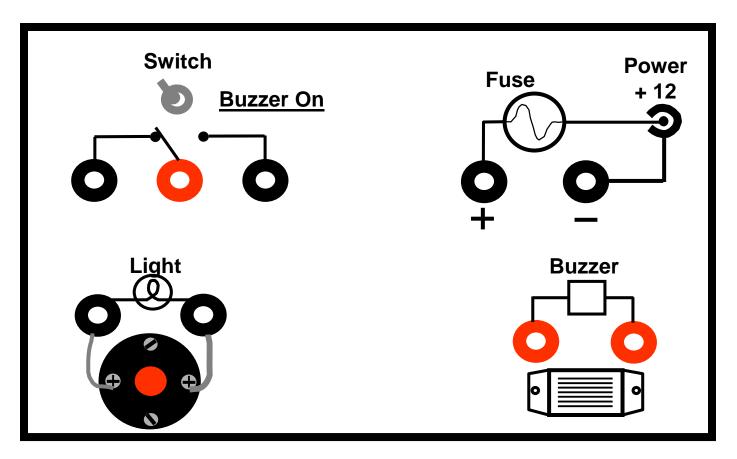Direct Current Test Box Draw Circuit to Switch Buzzer On / Off - Instructor draws this one first




Direct Current Test Box

Draw Circuit to Switch Light On / Off

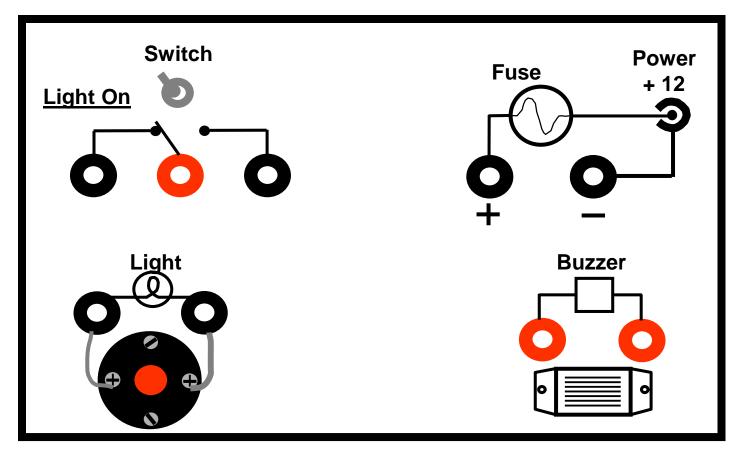


Direct Current

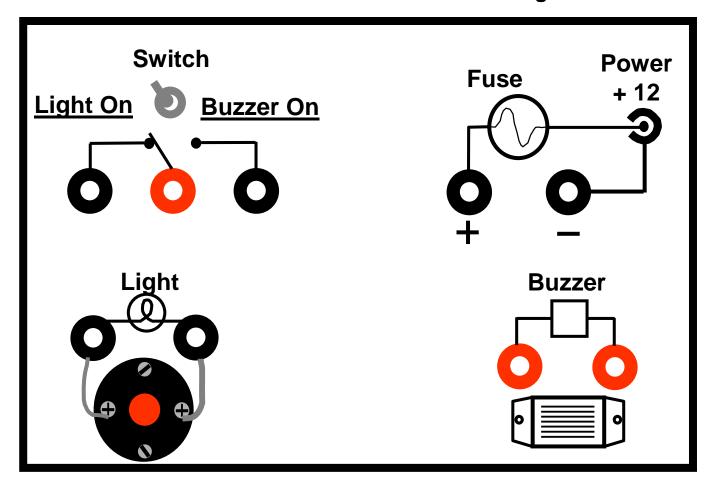
Draw Circuit to Turn Buzzer on in one Direction and Light in other Direction



Two Switches Control One Light

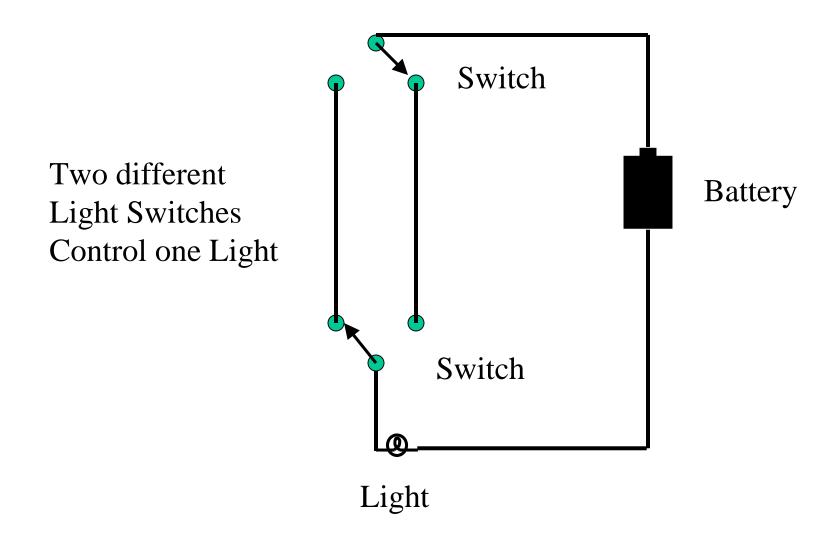


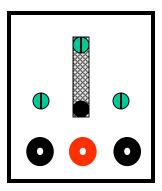Draw a Circuit with Two Switch External Switch and On-board Switch



When complete dismantle switch box and put all components back into its box.

Turn Light on

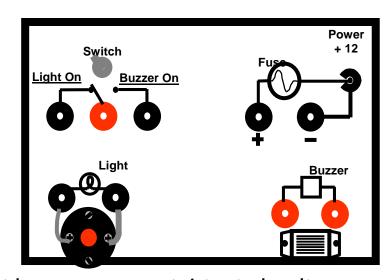

Pass out boxes, connect 4 test circuits Students work at own pace