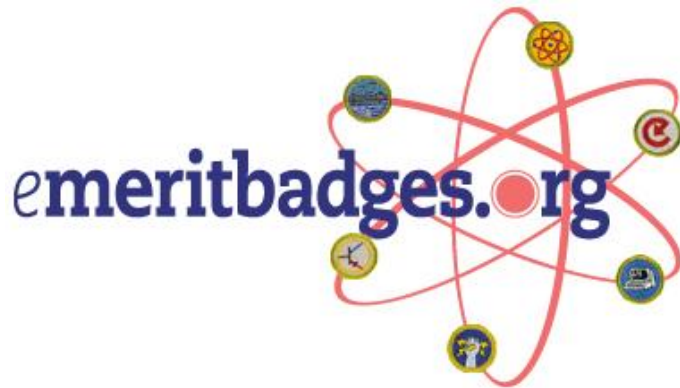





# Electronics Merit Badge

## Class 2



# Resistance

- Resistance is an electrical property of a material that “resists” the flow of electrons.
- The schematic symbol for a resistor is: 
- Common units for resistance are:
  - Ohms
  - Kilohm: 1K= 1000 ohms, 10K = 10,000 ohms
  - Megohm: 1M = 1,000,000 ohms
- The units symbol for ohms is:  $\Omega$  (ohms)



# Current

- Current: Defined as “flow of electrons”.
- Current: Units of current is AMPS.
- Current: Electrical symbol for current is I.
- Common units for current are:
  - Amps
  - Milliamps (ma):  $1 \text{ ma} = .001 \text{ amp}$
  - Microamps (ua) :  $1 \text{ ua} = .000001 \text{ amp}$ , or  $.001 \text{ ma}$
  - Nanoamps (na) :  $1 \text{ na} = .000000001 \text{ amp}$  or  $.000001 \text{ ma}$ , or  $.001 \text{ ua}$ .



# Voltage

- Volts is the electrical force that causes electrons (current) to flow.
- Units of volts is VOLTS.
- The symbol of volts is E or V. We will use V.
- Common units for voltage are:
  - Volts
  - Millivolt (mv) : .001 volt.
  - Microvolt (uv) : .000001 volt, or .001 mv
  - Nanovolt (nv) : .000000001 volt, or .000001 mv, or .001 uv.



# Ohms Law

- One of the most important laws in electronics/electricity.
- $V = I \times R$  : Voltage = Current x Resistance
- Volts is measure in VOLTS, current is measured in AMPS, and resistance is measured in OHMS.
- 1 AMP, going through 1 OHM of resistance, generates a voltage drop of 1 VOLT.
- $1 V = 1 A \times 1 \Omega$ .




# More Ohm's Law

Different forms of Ohm's Law:

$V = I \times R$  : Voltage = Current X Resistance

$I = V / R$  : Current = Voltage / Resistance

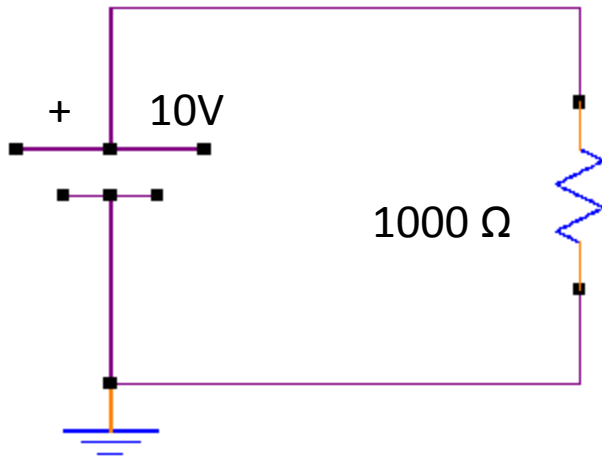$R = V / I$  : Resistance = Voltage / Current



Volts = 10.

Resistance =  $1000\Omega$

Compute current.

$I = V / R$

$I = 10 / 1000 = .01A$

$.01A = 10ma$

Question: what would the current be if the voltage was 1 V? How about 1000 V?




# Ohm's Law Exercise

- Using a meter, we will measure some resistors.
- Then, using ohm's law, we will calculate the resistor's values. To do this, we will use the meter to measure current and voltage in a circuit.



# Ohms Law – Step 1

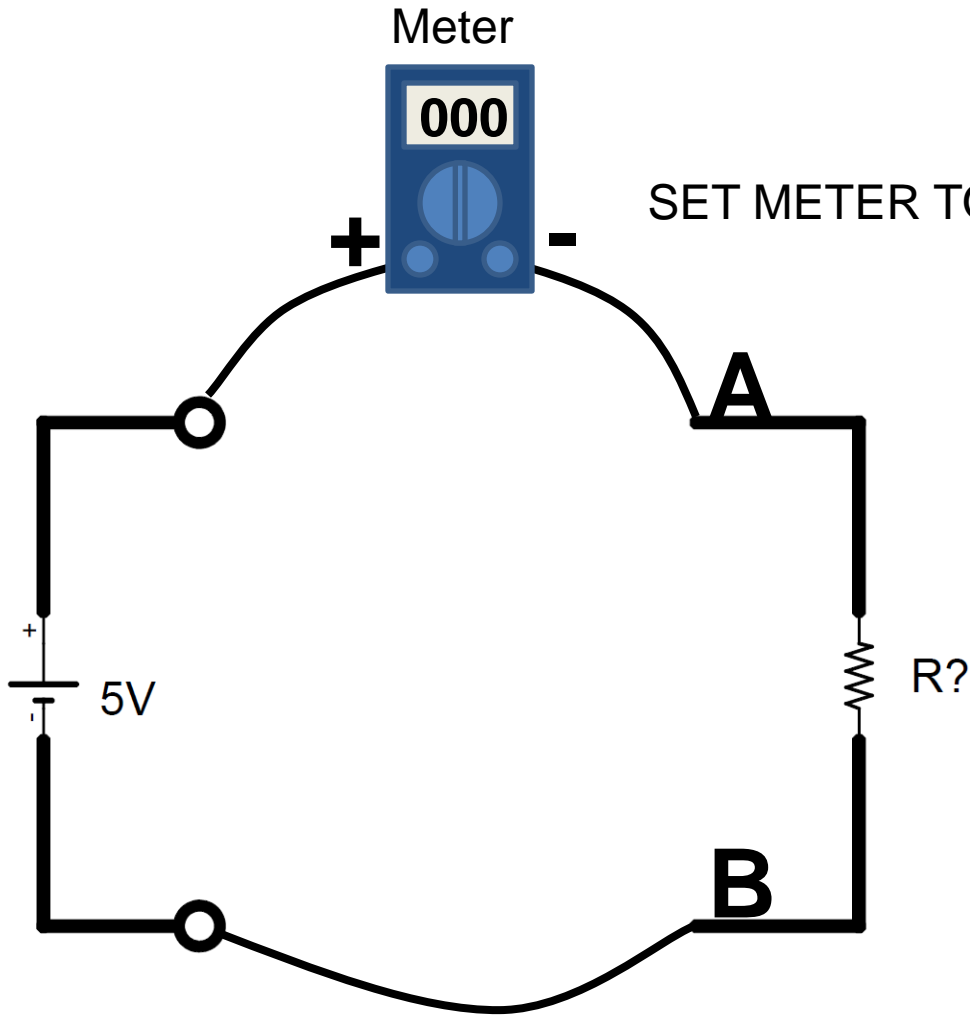

SET METER TO DCA -20m


Using the meter,  
measure current.

$I =$  \_\_\_\_\_ amps





# Ohms Law – Step 2

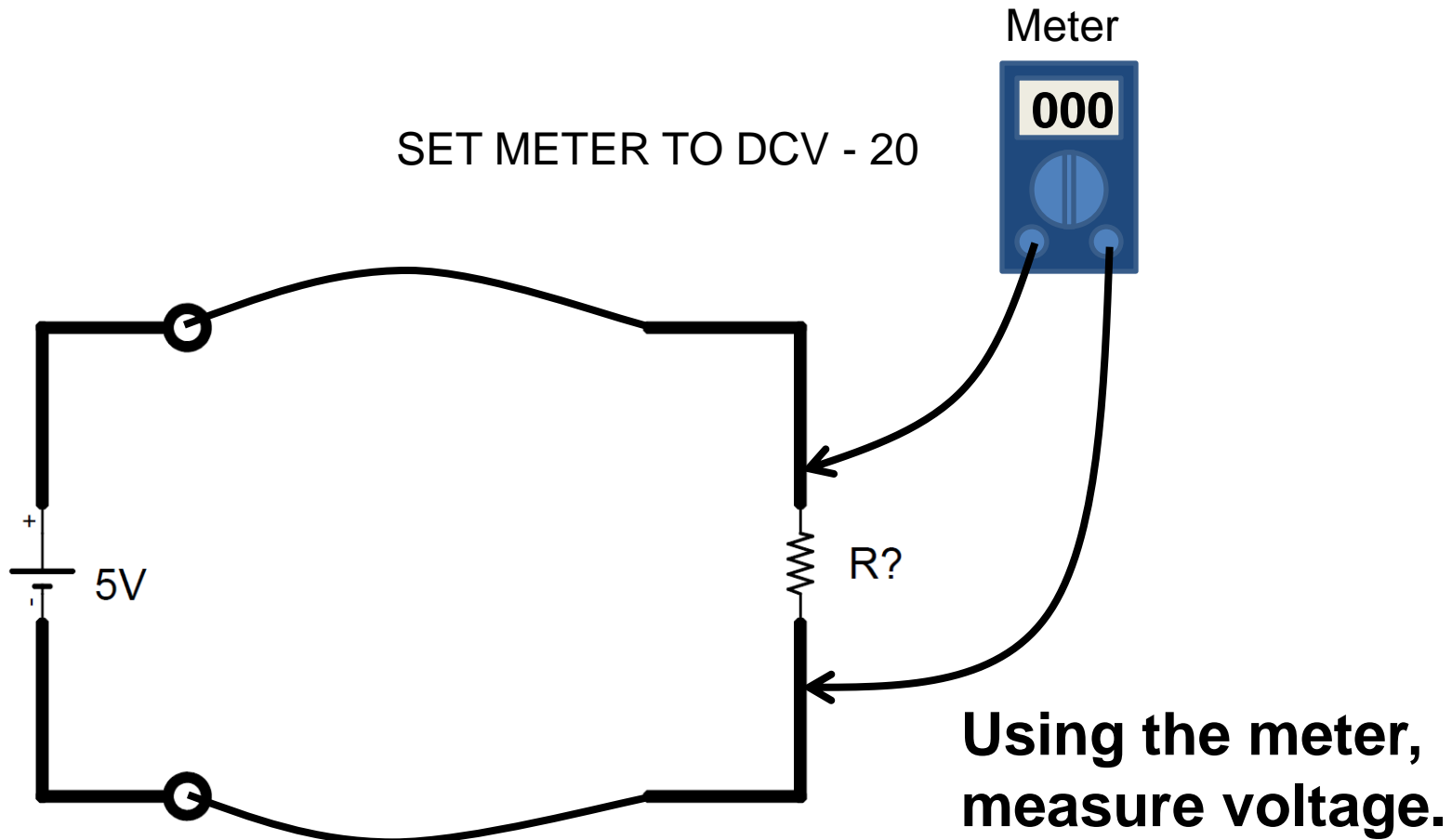

V = \_\_\_\_\_ volts



# Ohms Law – Step 3

**Calculate resistance from your 2 measurements.**

**Ohms Law :  $V = I \times R$ .**


Therefore,  **$R = V / I$**  <- Use this equation.

**Note: you will be measuring current on the 20ma range, so a value of 2.5ma needs to be written as .0025A when using this equation.**



# Ohms Law – Step 4

SET METER TO  $\Omega$  – 20k

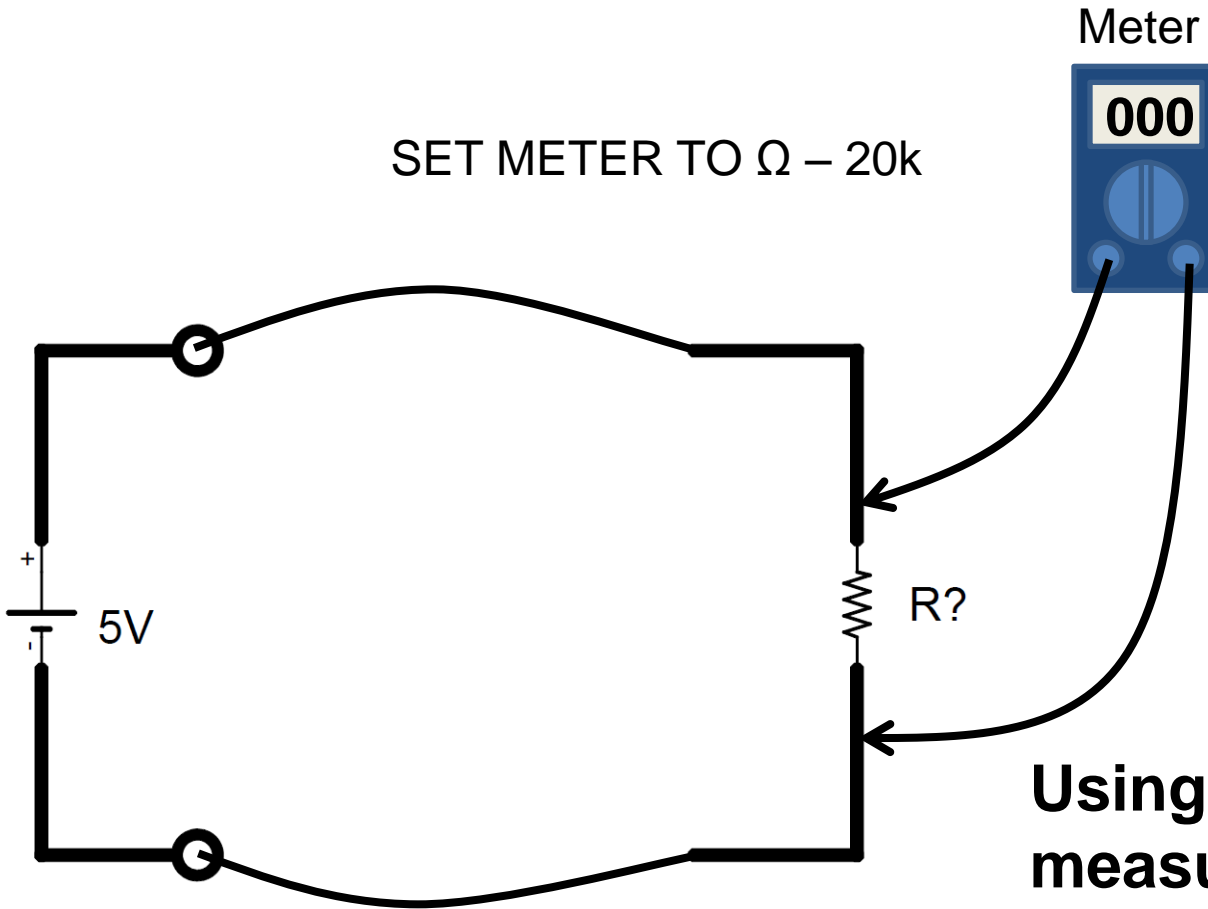

Using the meter,  
measure Resistance.

R = \_\_\_\_\_ ohms

How does this compare with your calculated value?

